

Analog lab

Exp - I

Venkata Subhash M.
23F3000773

I. expression for amplitude of V_m :-

The comparator switches its state when voltage at +ve terminal of it is greater than V_{cm} .

E) the ratio $\frac{R_2}{R_3}$ controls the voltage swing of V_{ramp} .

→ for voltage divider;

let's say $V_{cm} + V_m/2$ is the max V_{ramp} attains & $V_{cm} - V_m/2$ is the min V_{ramp} reaches.

$$V_{ramp} = V_{cm} \pm \left(\frac{R_2}{R_3}\right)V_{cm}$$

Hence, Peak to Peak amplitude of V_m is:-

$$V_m = 2 \left(\frac{R_2}{R_3}\right)V_{cm}$$

II Deriving the oscillation Freq F_{sw} :-

→ Freq. depends on current thru the capacitor.

From,

$$I = \frac{V_{sqr} - V_{cm}}{R_1}$$

$$= C_1 \frac{dV_{ramp}}{dt}$$

$$e) \frac{dV_{ramp}}{dt} = \frac{V_{sqr} - V_{cm}}{R_1 C_1}$$

Integrating... & time period is $\frac{T_{sw}}{2}$

$$e) V_m = \left(\frac{V_{sqr} - V_{cm}}{R_1 C_1} \right) \times \frac{T_{sw}}{2}$$

∴ ramp
switches
at every
 $T_{sw}/2$

$$T_{sw} = \frac{2 R_1 C_1 V_m}{V_{sqr} - V_{cm}} \quad \left(\because V_m = 2 \left(\frac{R_2}{R_3} \right) \cdot V_{cm} \right)$$

$$T_{sw} = \frac{4 R_1 C_1 V_{cm} \left(\frac{R_2}{R_3} \right)}{V_{sqr} - V_{cm}}$$

$$\text{If } V_{sqr} = V_{DD} \text{ \& } V_{cm} = \frac{V_{DD}}{2}$$

$$T_{sw} = \frac{4 R_1 R_2 C_1}{R_3}$$

$$e) F_{sw} = \frac{1}{T_{sw}} = \frac{R_3}{4 R_1 R_2 C_1}$$

Values used:-


R1- 25K

R2- 1K


R3- 5K

C1- 10nF

LT spice Circuit:-

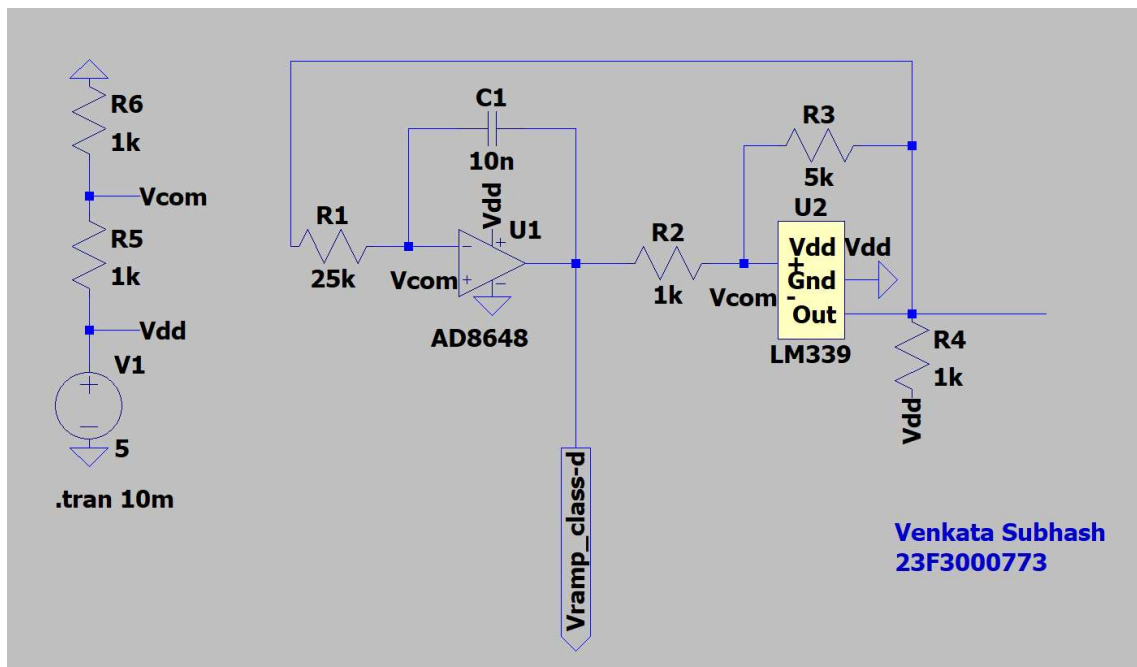

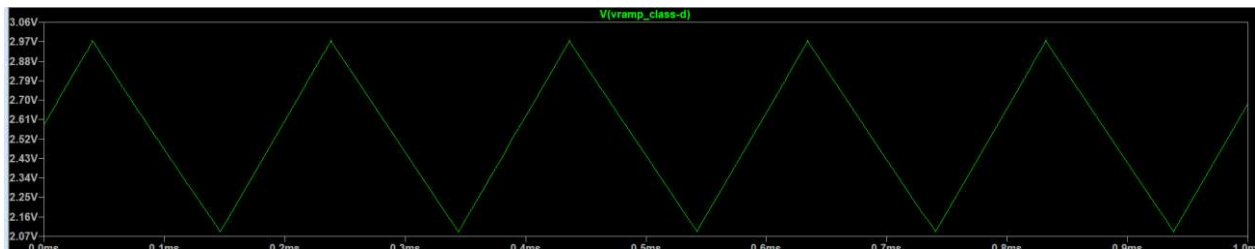MCP 6004 output (Ramp):- (Amplitude = 0.5v)



LM 339 output (square) :-

